



**PRINCETON
UNIVERSITY**


Inductor-Linked Multi-Output Switched-Capacitor Power Architecture for High Current Chiplets

*Mian Liao⁺, Daniel Zhou⁺, Ping Wang, Minjie Chen
Department of Electrical and Computer Engineering
Andlinger Center for Energy and the Environment
Princeton University*


⁺M. Liao and D. Zhou contributed equally to the paper and the presentation



 
Power Delivery Challenges of High Current Chiplets



Chiplets

 



3D-IC

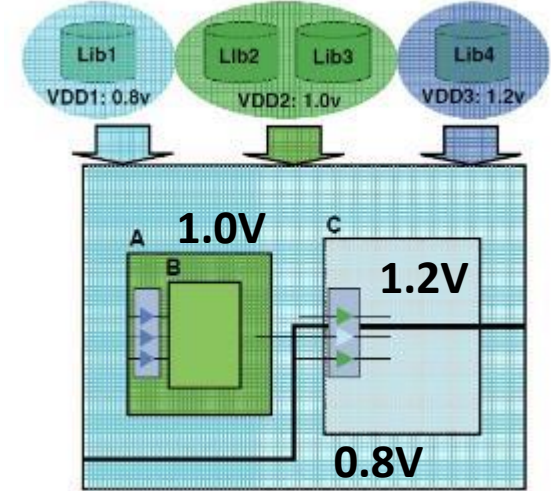

- High power, higher input voltage (48 V), lower output voltage (<0.5 V)
- Multiple individually regulated output voltages: 0.8V, 1.8V, 3.3V, etc.
- Significant variation in bus voltage (>40%) due to complicated PDN
- Sophisticated voltage regulation requirements: dynamics, ripple, noise
- Efficiency, power density, packaging, signal/power integrity

Power Delivery Solutions for Chiplet Systems

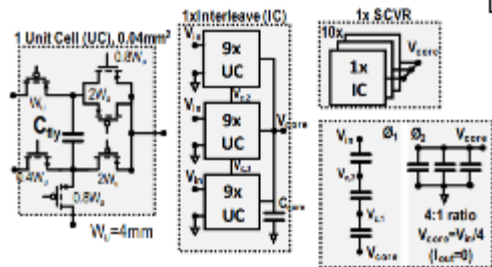 Low Power Low Conversion Ratio Capacitor-based



IntAct: Off-chip VRM + in-substrate SwCap


- Input: 0.9V to 2.9V
- Output: 0.4V to 1.8V
- Power: 2.6W

P. Vivet *et al.*, "IntAct: A 96-Core Processor With Six Chiplets 3D-Stacked on an Active Interposer With Distributed Interconnects and Integrated Power Management," in *IEEE Journal of Solid-State Circuits*, vol. 56, no. 1, pp. 79-97, Jan. 2021.

High Power High Conversion Ratio Inductor-based



Tesla Dojo

 

MPS Vertical Power Module


- Input: 4V to 16V
- Output: 0.5V to 1V
- Current: 120A




MPC22161

High Conversion Ratio Hybrid SwCap Multi-Output Designs

Capacitors : high density, high Q

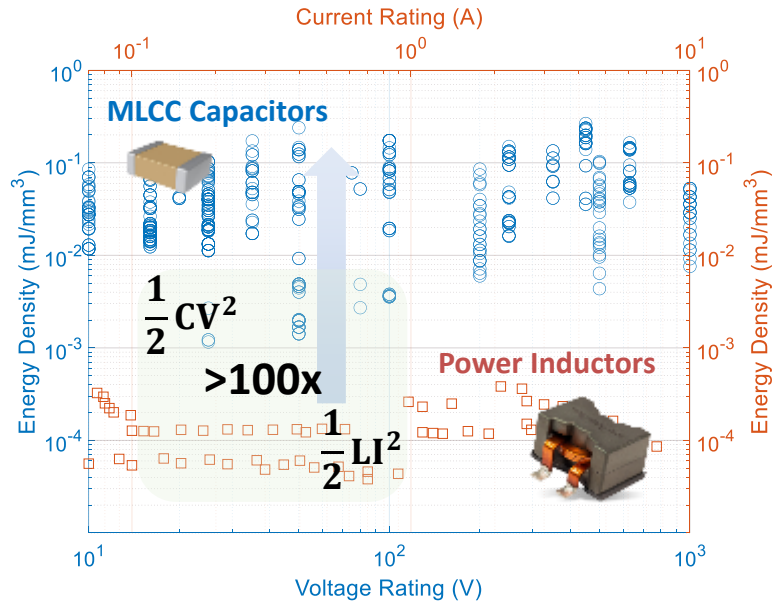

 
Magnetics : design flexibility & functionality



- Sullivan et al., "On Size and Magnetics: Why Small Efficient Power Inductors are Rare," 3D-PEIM'16.
- Sullivan and Chen, "Coupled Inductors for Fast-Response High-Density Power Delivery: Discrete and Integrated," CICC'21.
- Kyaw et al., "Fundamental Examination of Multiple Potential Passive Component Technologies ...," TPEL'18.


DC Intermediate Bus versus AC Intermediate Bus

Two-Stage Design with Capacitor-Link

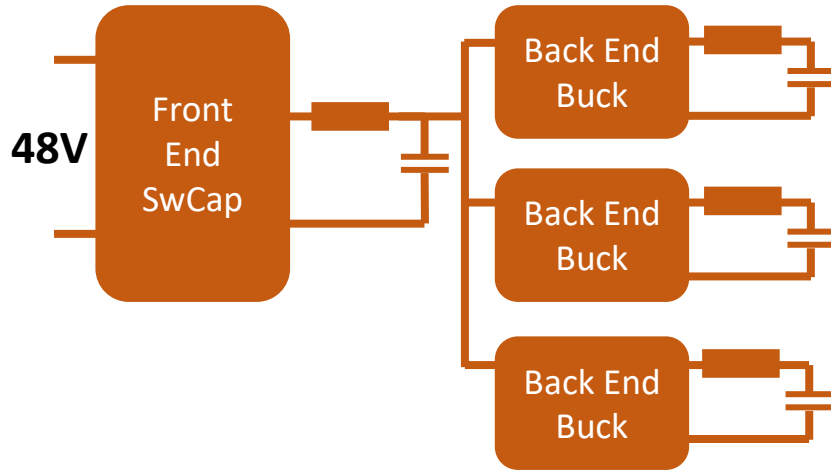


- 1) Need on-chip inductors
- 2) Large bus capacitor & inductor
- 3) Tightly regulated intermediate bus

Two-Stage Design with Inductor-Link

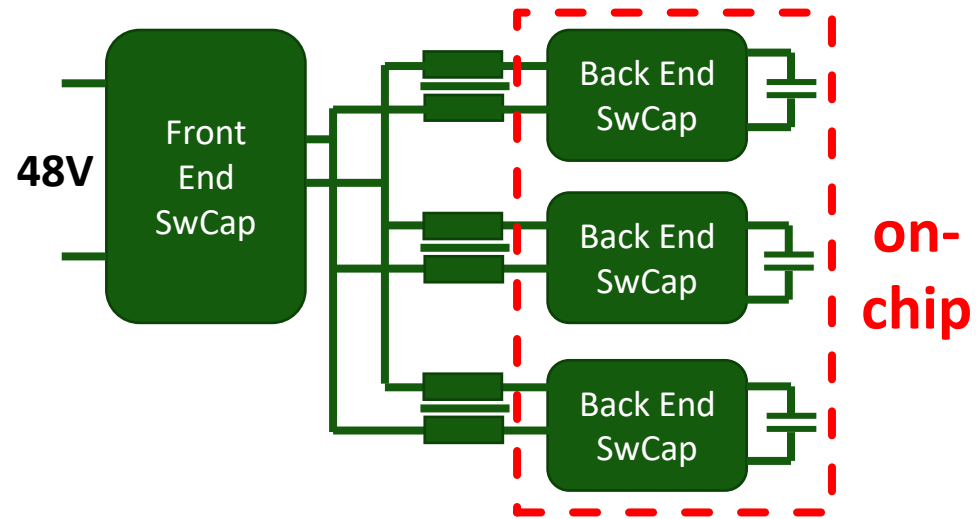

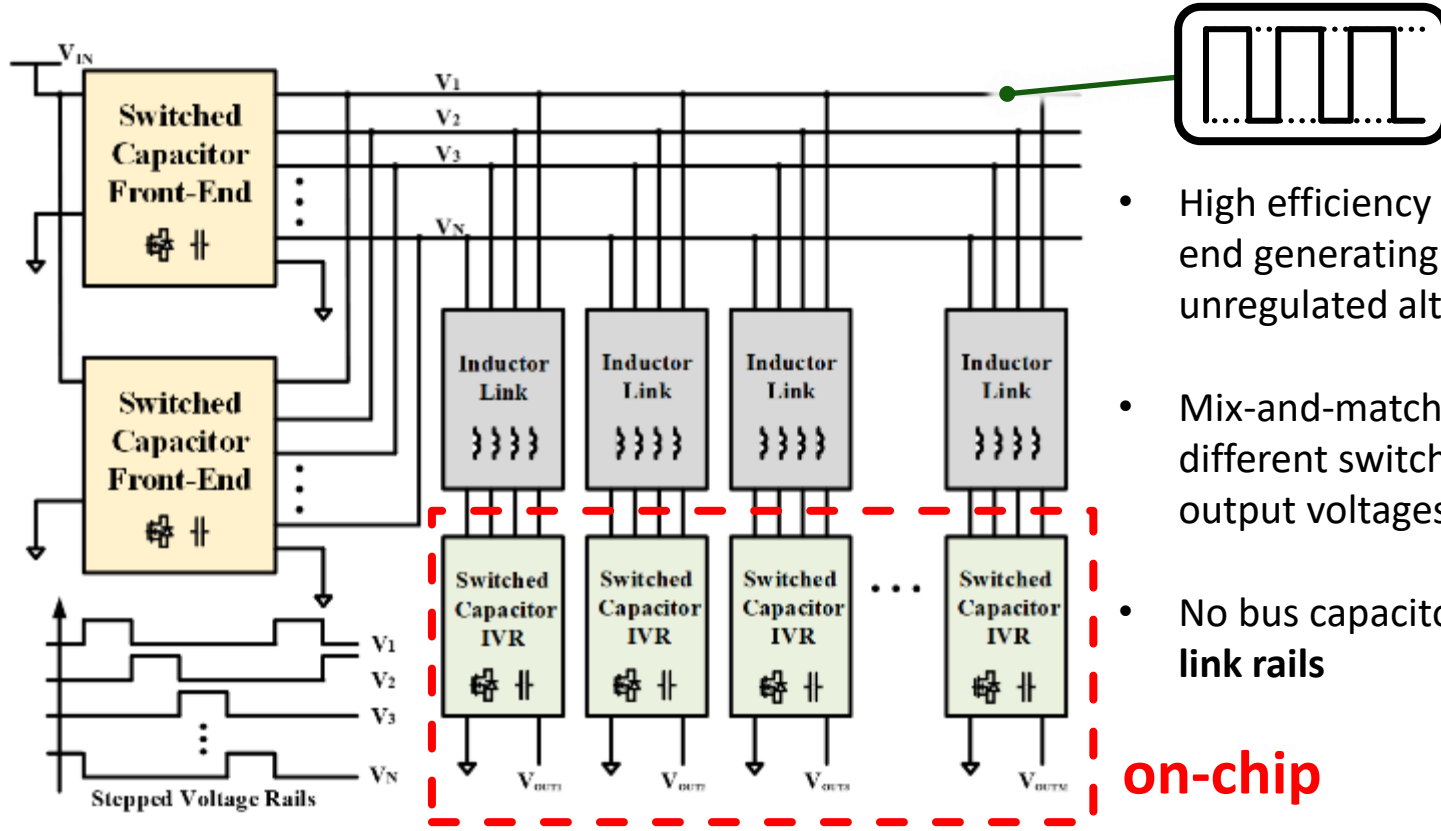- 1) Integrated back-end w/ on-chip capacitors
- 2) No bus capacitor, coupled inductor links
- 3) Unregulated intermediate bus

Modular Building Blocks for the Inductor-Link Architecture




- High efficiency soft-charged front end generating multiple interleaved, unregulated alternating bus voltages
- Mix-and-match output stages with different switching frequencies and output voltages
- No bus capacitors, multiple **inductor-link rails**

on-chip

“Inverter-Rectifier” Architecture

“Power lines”

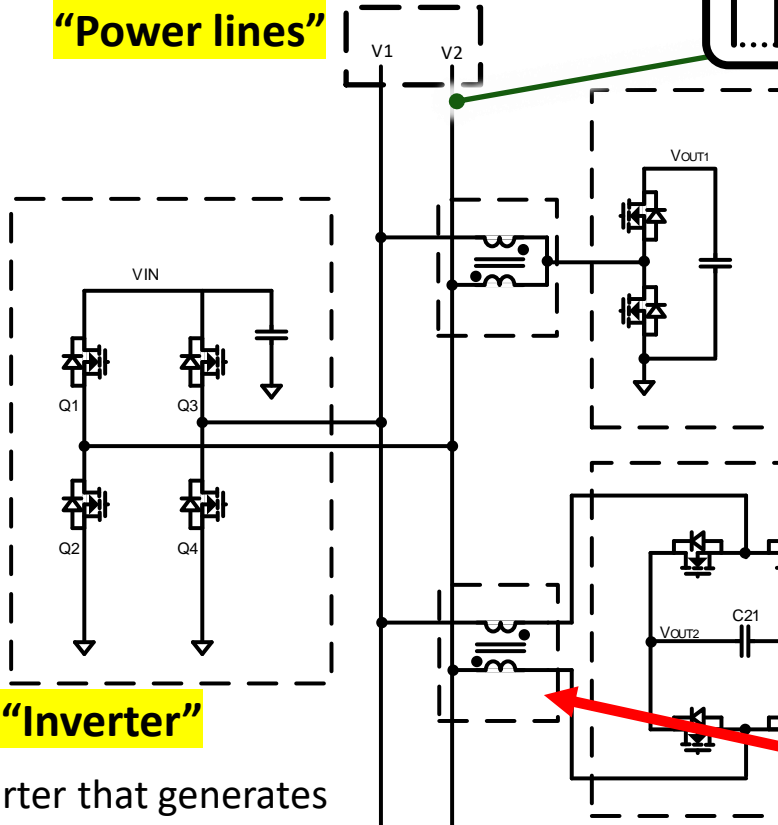

SwCap “Rectifier”

A converter that “smooths” pulsed voltage


SwCap “Inverter”

A converter that generates pulsed voltage

Leverage high density capacitors close to Chiplet or on-chip

Leverage current smoothing inductor off-chip

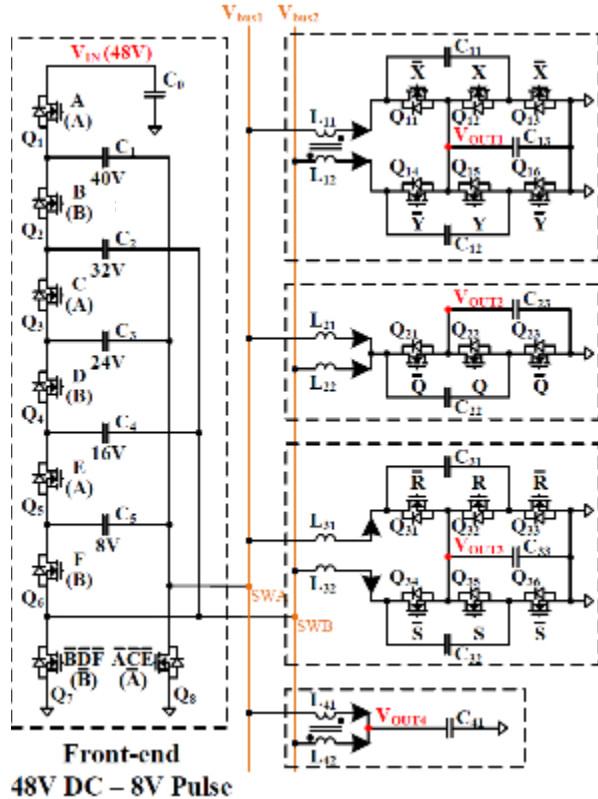Example Implementation of the Inductor Link Architecture



- Front-end: Dickson-like step-down architecture
- Back-end: Inductor-link switched cap rectifier

Front end:


- Efficiently convert 48V into pulsed 8V rail voltage
- Average rail voltage between 0V and 8V

Back end:

- Convert pulsed rail voltage into regulated dc voltage
- Output voltage between 0V and average rail voltage

Front end and back end separately controlled and separated regulated. One front-end can be loaded by multiple back-ends with different power handling capability.


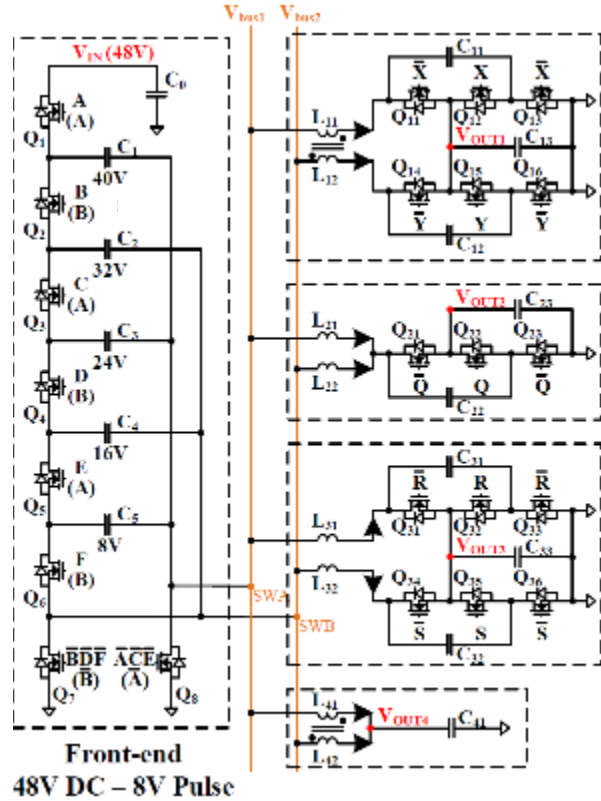
Example Implementation of the Inductor Link Architecture




Multiple switching implementations are possible

Hard-charging


Soft-charging

  

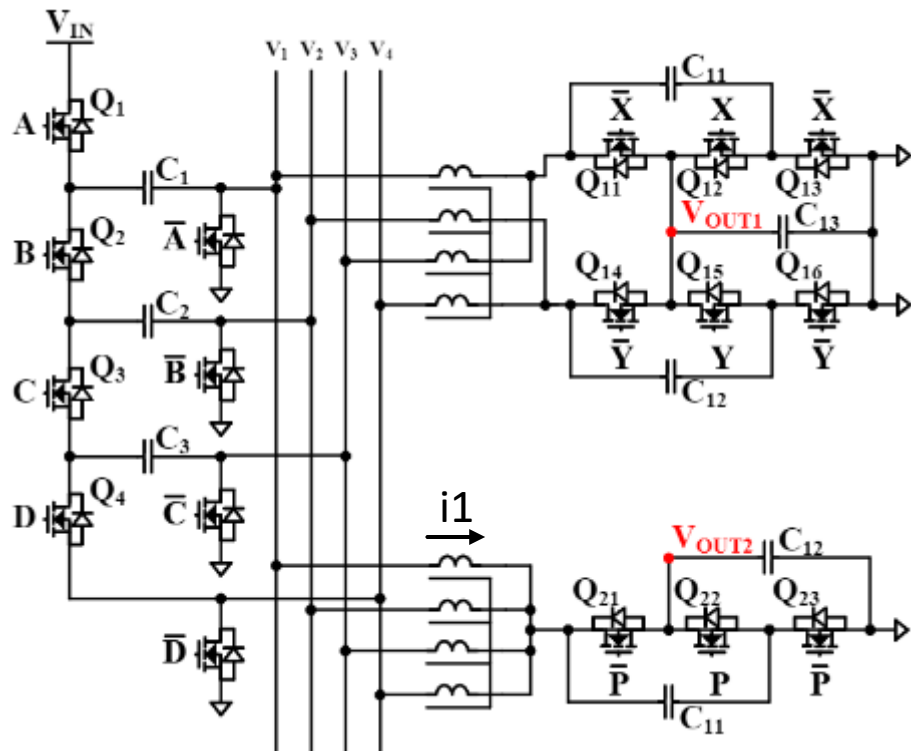Multi-Rail Implementation with Full Soft Charging





4 x Interleaved Voltage Rails

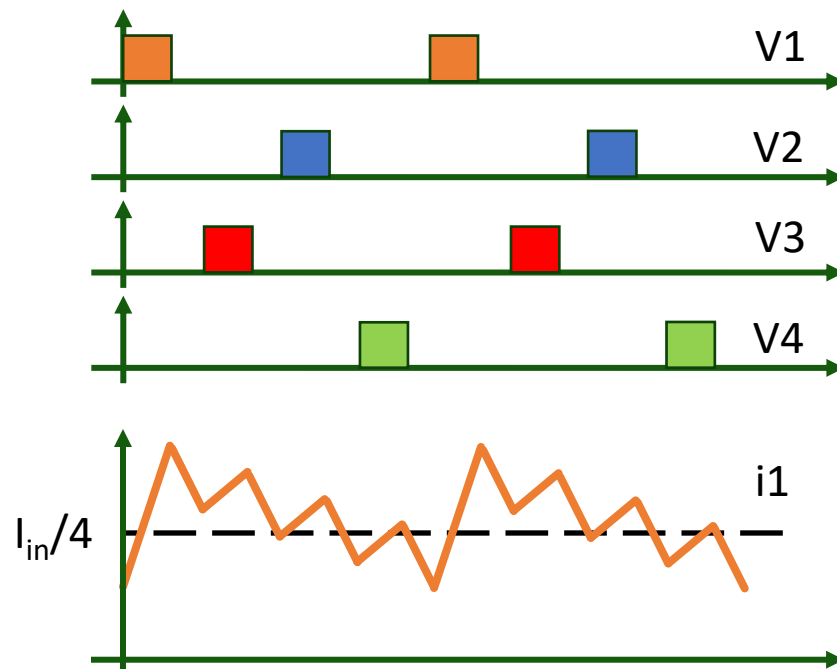

- Fully soft-charged front end, higher power delivery capability, smaller current ripple

3D Packaging Concept for the Inductor-Link Architecture

  

Requirements 48V-1V >1A/mm² <7 mm height 500A~1000A 5A/ns 90%

Conversion Ratio




Area Density

Power/Signal/Thermal

Transient

Efficiency

On-Chip / In-substrate Coupled Inductor

   

Air Core INTEL



Inductor Metric	Composite Core (This Work)	Air Core Inductor [2]
Inductance	2.5 nH	1.2 nH
DC Resistance	12 mΩ *	7 mΩ *
I_{max}	8 A	8 A
L/R_{dc}	208 nH/Ω *	171 nH/Ω *
Area	0.4 mm ²	2 mm ²
Current Density	20 A/mm ²	4 A/mm ²
Energy Density	200 nJ/mm ³	19.2 nJ/mm ³
Peak Q (Freq)	33 (90 MHz) *	24 (140 MHz) *




- Bharath, K., Radhakrishnan, K., Hill, M. J., Chatterjee, P., Hariri, H., Venkataraman, S., . . . Srinivasan, S. (2021, 1 June-4 July 2021). Integrated Voltage Regulator Efficiency Improvement using Coaxial Magnetic Composite Core Inductors. Paper presented at the 2021 IEEE 71st Electronic Components and Technology Conference (ECTC).

Prototype System Implementation

Cascaded Boot-strap Gate Drive Circuits

 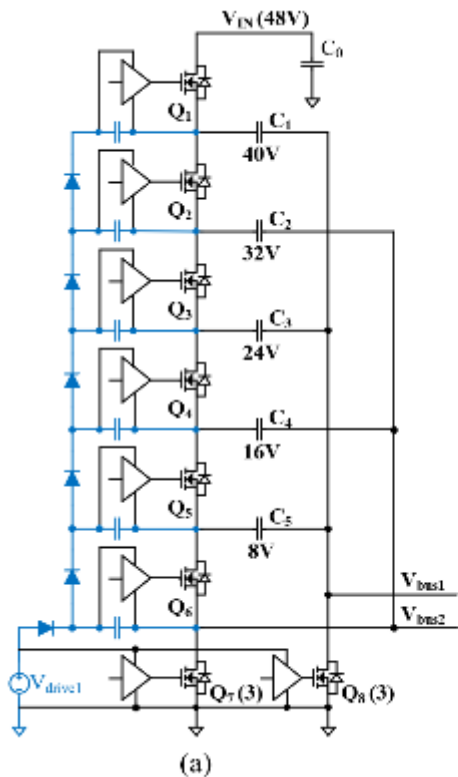


Front-End

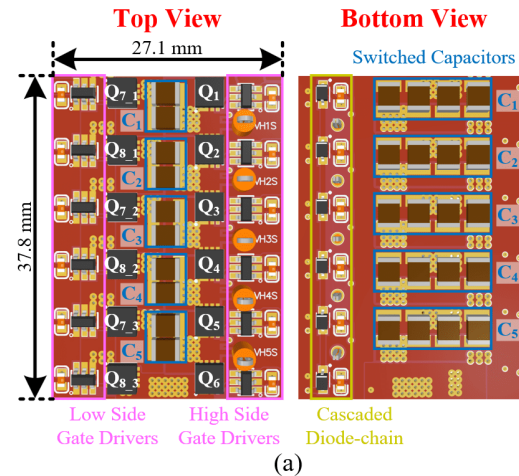


Back-End




Eaton CL1208
Coupled Inductor

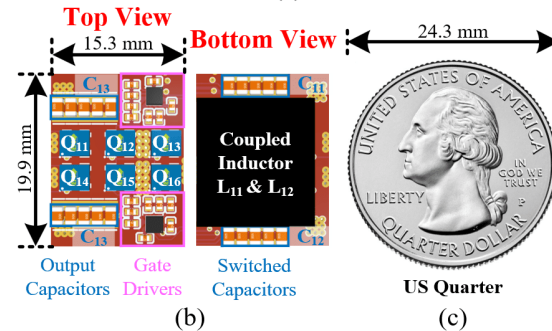

Operation Waveforms

 

 
48 V to 2 V average bus voltage, 252.5 kHz front-end frequency with hard-charging pattern




48-V to 1.3-V/140A in hard-charging mode with 72-ft³/min air flow from the bottom.

Measured Efficiency

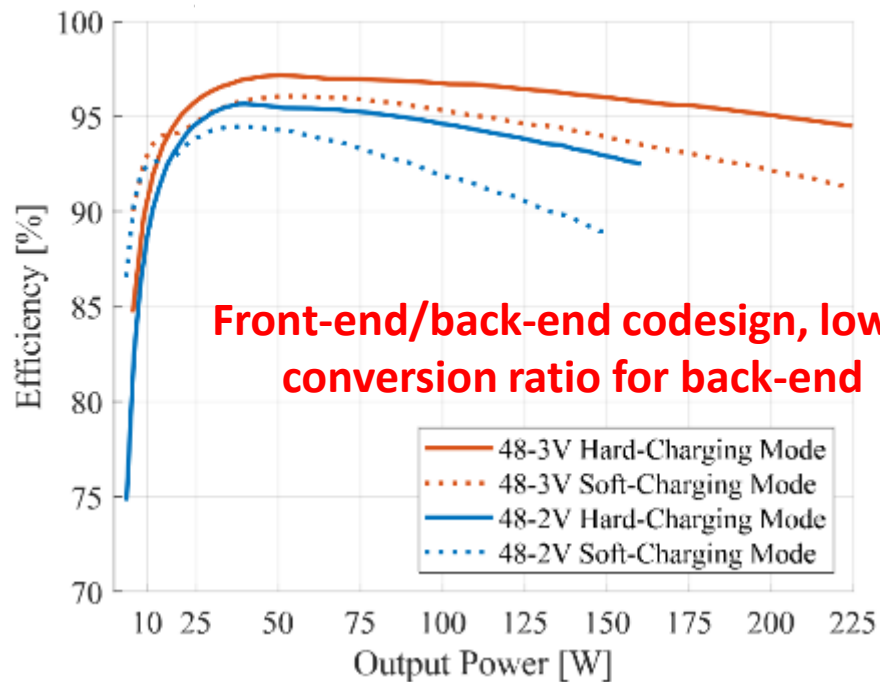
High efficiency front-end inverter stage:



Full architecture efficiency:

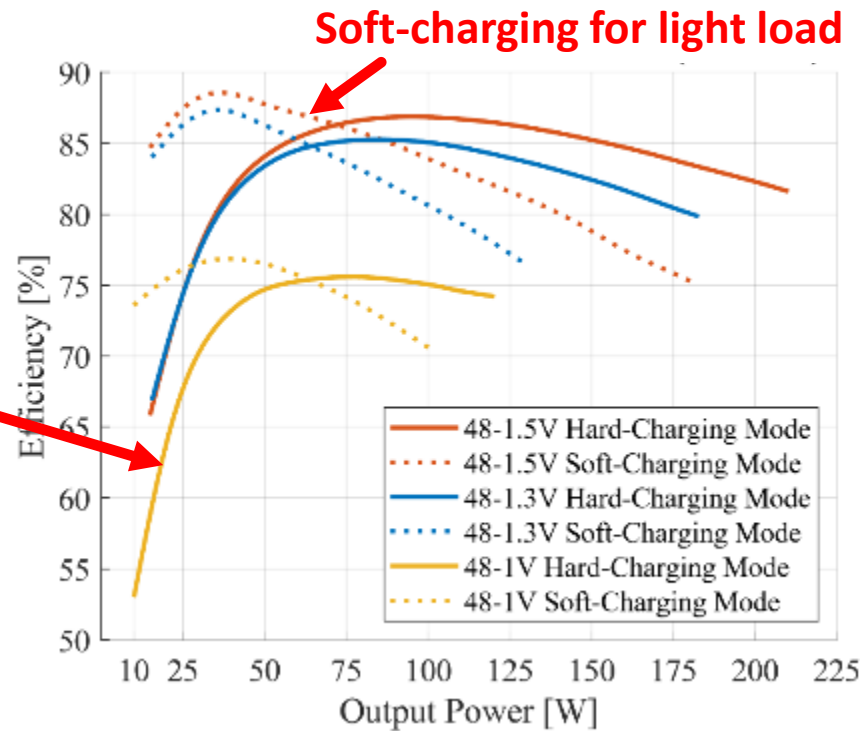


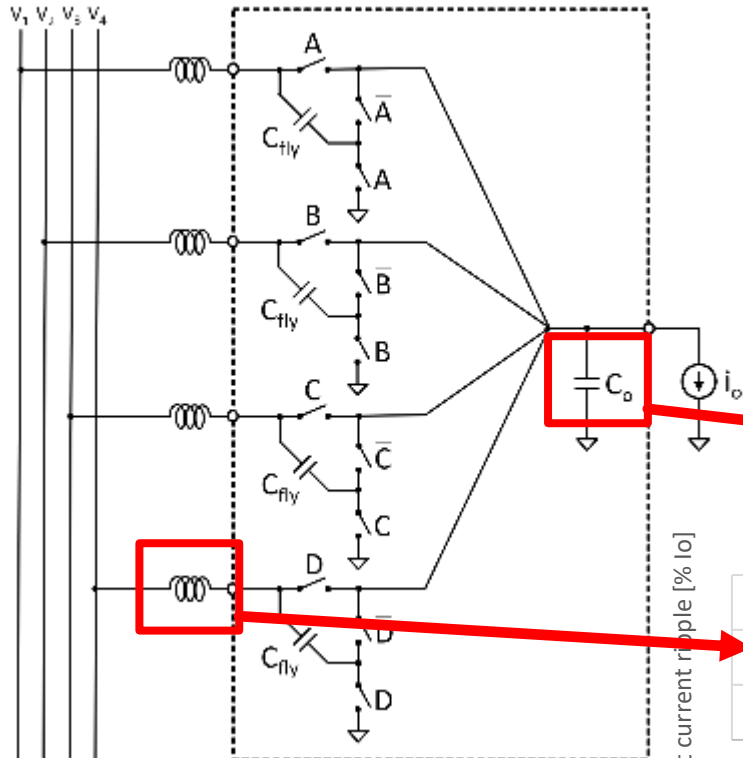
Design Considerations of the Switch-Cap Rectifier



Input: 8V pulsed at 22.5% duty cycle, 250~1000 kHz
 Output: 1V to 1.5V (20% to 80% duty cycle)
 Target: 10mV output ripple at 50 A output

First and second stage codesign:

  - First stage provides unregulated pulsed voltage, but current ripple should be small
- Min. bus voltage for higher second stage duty cycle




On-chip four-phase SwCap

Design Considerations of the Switch-Cap Rectifier


Capacitors determine loss and v_o ripple

- Off-chip caps: ESR @ $f_{sw} = 10 \text{ MHz} \gg$ switch $R_{ds(on)}$
- If caps have low ESR (e.g. on-chip), charge sharing dominates loss and ripple

“Slow switching limit” (high ESR caps)

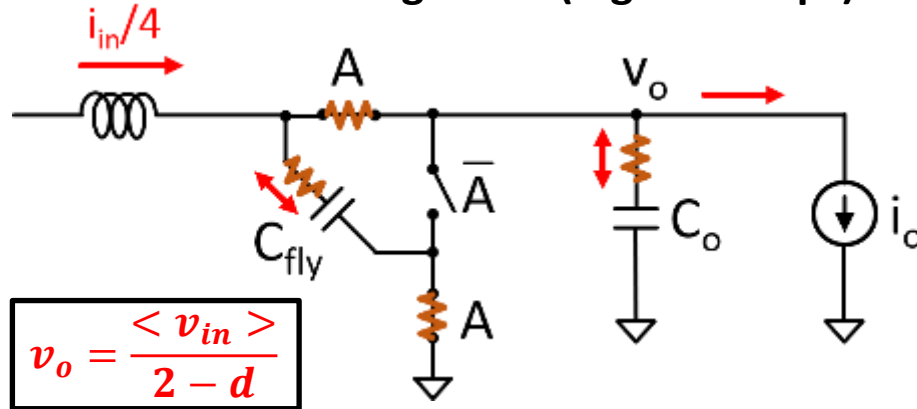


“Fast switching limit” (low ESR caps)

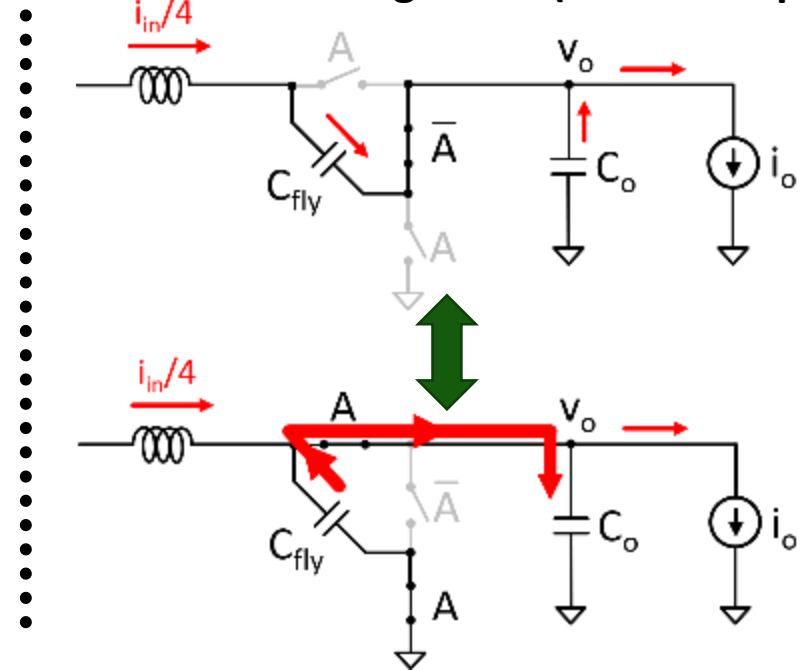


M. D. Seeman and S. R. Sanders, "Analysis and Optimization of Switched-Capacitor DC-DC Converters," in *IEEE Transactions on Power Electronics*

Design Considerations of the Switch-Cap Rectifier


Total Predicted Loss

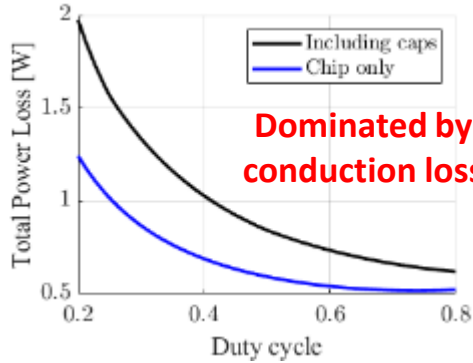

Loss Breakdown

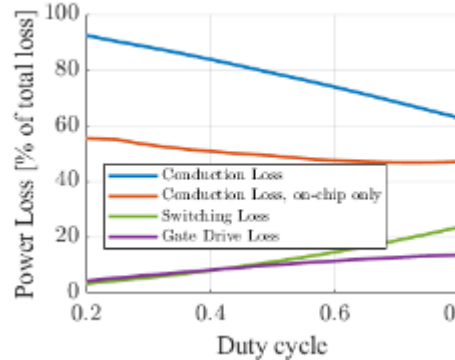

Predicted Ripple

 

Process: 180 nm, 1.8V NMOS


Chip size: 3mm * 3mm

C_{fly} (per-phase) = 26 uF


C_o (total) = 47 uF

Switch $R_{ds(on)}$ = 0.5/1 mΩ


Capacitor ESR = 0.9/0.3 mΩ

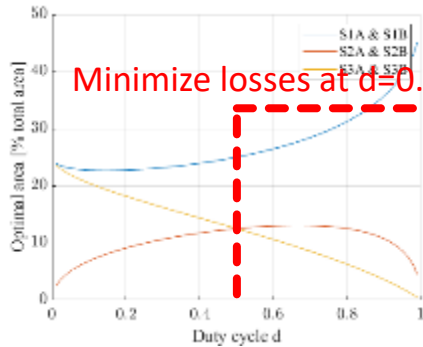


Chip, 9mm²

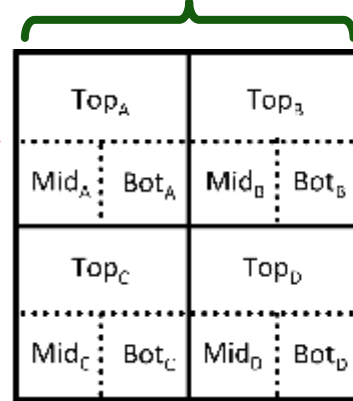

Flying caps, 12 mm²

 


Output caps, 9mm²

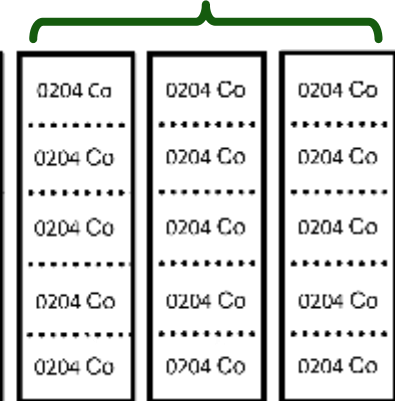

Conclusion

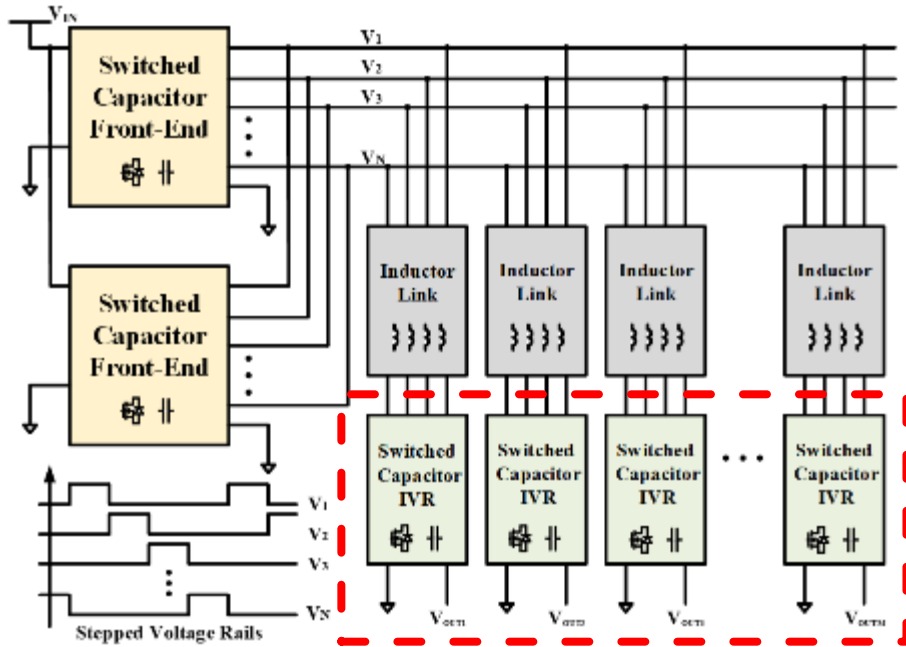48V Chiplet power delivery architecture with inductor link and multiple outputs



on-chip

